IIT-JEE/NEET-PHYSICS

AC

1

2

The equation of an alternating current is $i = 50\sqrt{2} \times \sin 400\pi$ ampere then the frequency and the root mean square of the current are respectively

(b) 400 π Hz, $5\sqrt{2}$ amp (c) 200 Hz, $5\sqrt{2}$ amp (d) 50 Hz, 200 amp

$$i_{sinut} = \frac{1}{J_{z}} = \frac{$$

If the frequency of an alternating current is 50 *Hz* then the time taken for the change from zero to positive peak value and positive peak value to negative peak value of current are respectively

 $(a)^{1/200}$ sec, 1/ 100 sec (b)

1/ 100 sec, 1/200 sec (c) 200 sec, 100 sec(d)

SAFA

$$T = \frac{1}{50} \text{ SeC}.$$

$$T = \frac{1}{50} \text{ SeC}.$$

$$T = \frac{1}{200} \text{ SeC} \rightarrow 0 + 0 \frac{1}{10} \text{ Tr}_{2} \text{ SeC}$$

$$T = t = \frac{1}{200} \text{ SeC} \rightarrow 0 + 0 \frac{1}{10} \text{ Tr}_{2} \text{ SeC}$$

$$T = t = \frac{1}{200} \text{ SeC} \rightarrow 0 + 0 \frac{1}{10} \text{ Tr}_{2} \text{$$



$$i = 2 \sin (100 \pi F + \pi_3) = 2 \sin \pi_3$$

 $i = 2 \sin 6^\circ = \chi \times \sqrt{3} = 53 \text{ A}$



7

. 8

9

The voltage of an ac source varies with time according to the equation $V = 100 \sin(100\pi t) \cos(100\pi t)$ where *t* is in seconds and *V* is in *volts*. Then (a) The peak voltage of the source is 100 *volts* (b) The peak voltage of the source is 50 *volts*

(c) The peak voltage of the source is $100 / \sqrt{2}$ volts (d)The frequency of the source is 50 Hz

V= 1005in (100 Tt) LOS (100 Tt) 211 = 200 = 100HZ asino USO = Stazo Sin(100 Tt) cos(100 Tt) = 1/ sin (200 Tt) $V = 100 \times \frac{1}{2} \times \text{Sin}(200 \pi t) = 50 \text{Sin}(\frac{200 \pi t}{2})$

If the frequency of ac is 60 Hz the time difference corresponding to a phase difference of 60° is







(b) $1/\sqrt{2}$ (a) 1 (c) 100 (d) Zero In= Thein Th $P = ImVm \frac{103}{7} = 0$ T_{12} = Sinut T_{12} = Sinut T_{12} = S_{12} = S_{12} = S_{12} Po=1, m= 1/12.

The *r.m.s.* current in an ac circuit is 2 *A*. If the wattless current be $\sqrt{3}A$, what is the power factor



P= ImVm LOID

14





IIT-JEE/NEET-PHYSICS









A bulb of 60 volt and 10 watt is connected with 100 volt of ac source with an inductance coil in series. If bulb illuminates with it's full intensity then value of inductance of coil is (v= 60 Hz)

(b) 2.15 H

(d) 3.89 H

(a) 1.28 H (c) 3.27 H

27

IMP.

V1 = 80V ImXL = 80 .WL = 80













(b) 300 V, 2A
(c) 220 V, 2.2 A
(d) 100 V, 2A

39



In a series resonant *LCR* circuit, if *L* is increased by 25% and *C* is decreased by 20%, then the resonant frequency will

- (a) Increase by 10% (b) Decrease by 10%
- (c) Remain unchanged (d) Increase by 2.5 %



The self inductance of a choke coil is 10 mH. When it is connected with a 10V dc source, then the loss of power is 20 watt. When it is connected with 10 volt ac source loss of power is 10 watt. The frequency of ac source will be

- (a) 50 *Hz* (b) 60 Hz
- (c) 80 *Hz* (d) 100 *Hz*

40