
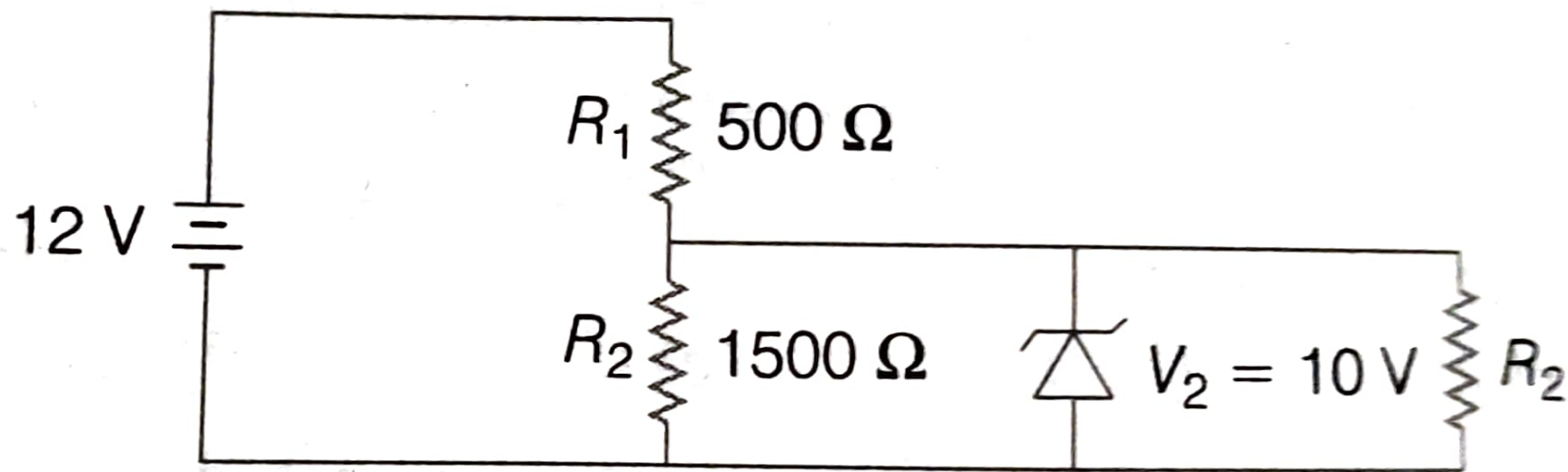


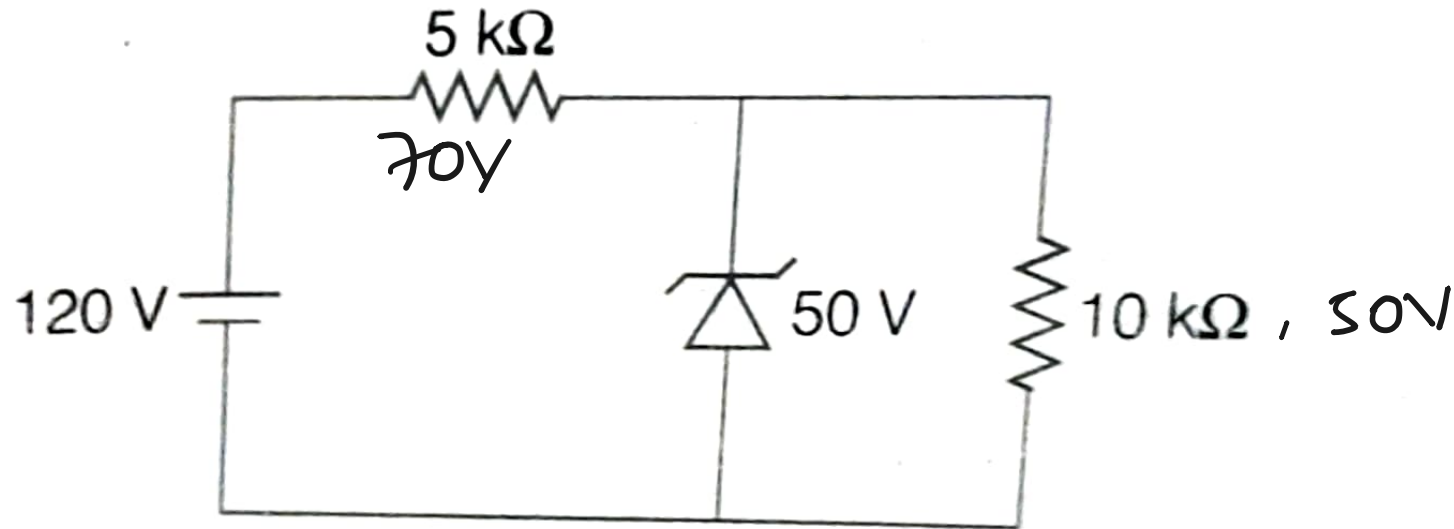12. In the given circuit, the current through zener diode is closed to
(Main 2019, 11 Jan I)




- (a) 6.0 mA (b) 6.7 mA (c) 0 (d) 4.0 mA

13. For the circuit shown below, the current through the Zener diode is
(Main 2019, 10 Jan II)



- (a) 14 mA (b) zero (c) 5 mA (d) 9 mA

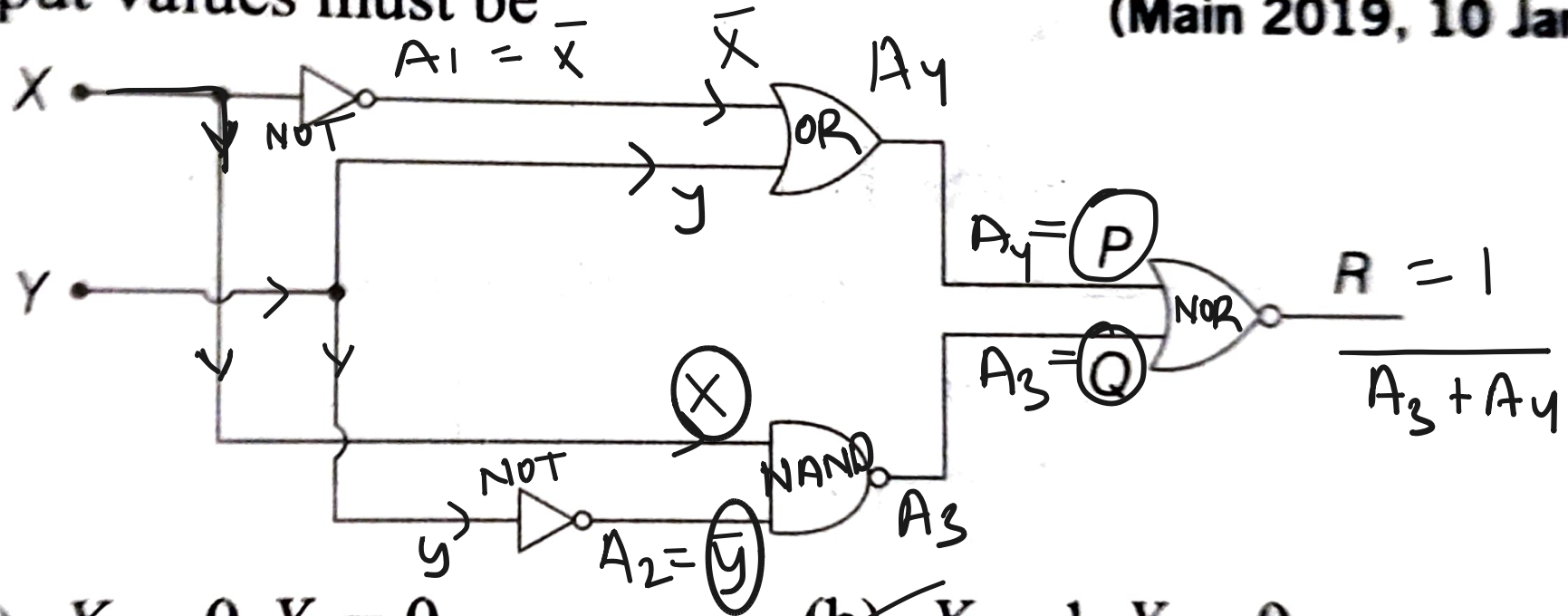- 14.** To get output '1' at R , for the given logic gate circuit, the input values must be (Main 2019, 10 Jan I)



- (a) $X = 0, Y = 0$
(c) $X = 1, Y = 1$

- (b) $X = 1, Y = 0$
(d) $X = 0, Y = 1$

$$A_1 = \bar{x}, A_2 = \bar{y}$$


$$A_3 = \bar{x} + y$$

$$A_3 = \overline{x \bar{y}}$$

$$Z = \overline{x \bar{y} + \bar{x} + y}$$


x	y	\bar{x}	$x\bar{y}$	$\overline{x\bar{y}}$	$\overline{x\bar{y} + \bar{x} + y}$
0	0	1	0	1	$\overline{1 + 1 + 0} = 0$
0	1	1	0	1	$\overline{1 + 1 + 1} = 0$
1	0	0	1	0	$\overline{0 + 0 + 0} = 1$
1	1				

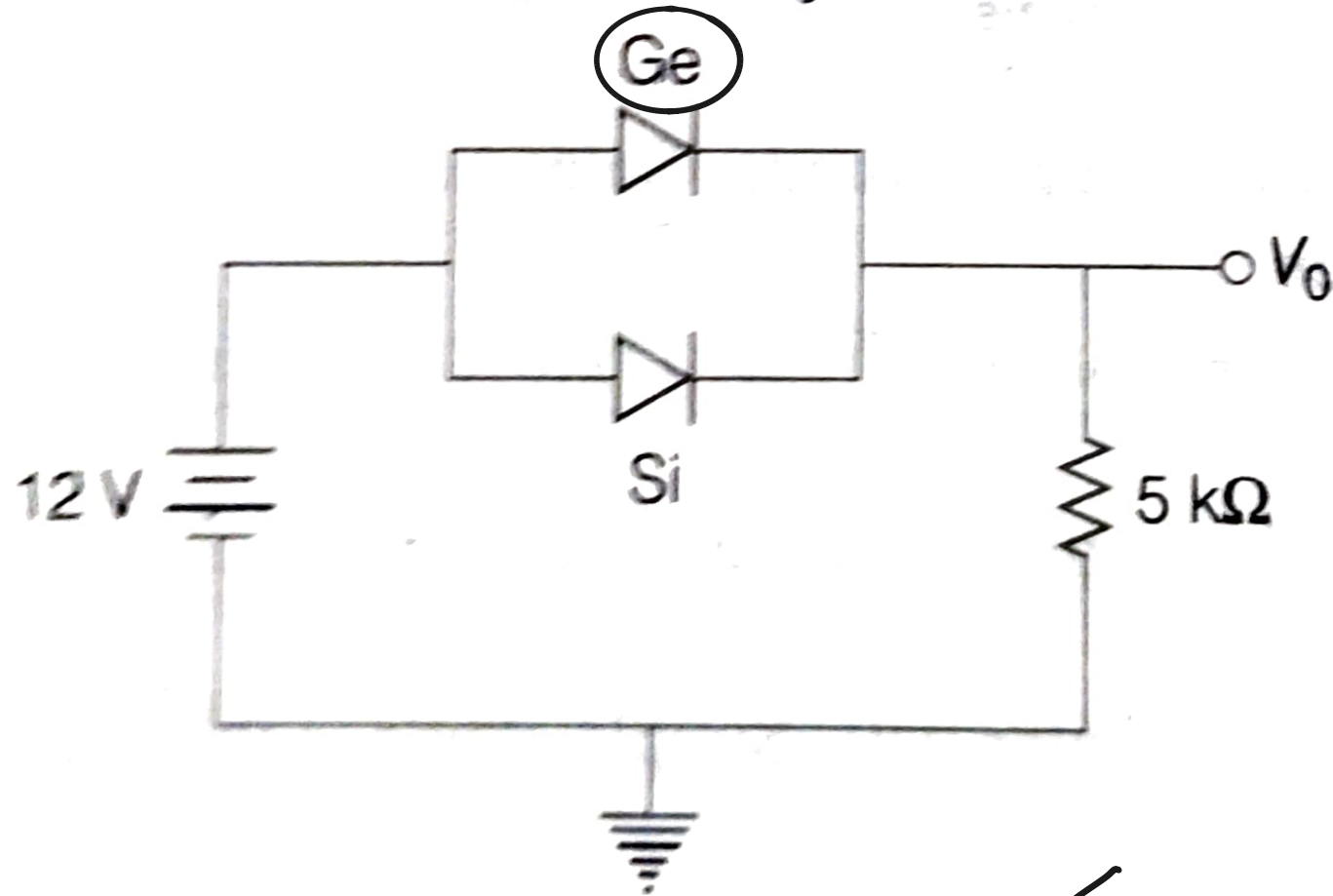- 15.** At 0.3V and 0.7V , the diodes Ge and Si become conductor respectively. In given figure, if ends of diode Ge overturned, the change in potential V_0 will be **(Main 2019, 9 Jan II)**




- (a) 0.2V (b) 0.6V (c) 0.4V (d) 0.8V

Case-1
initial out put.

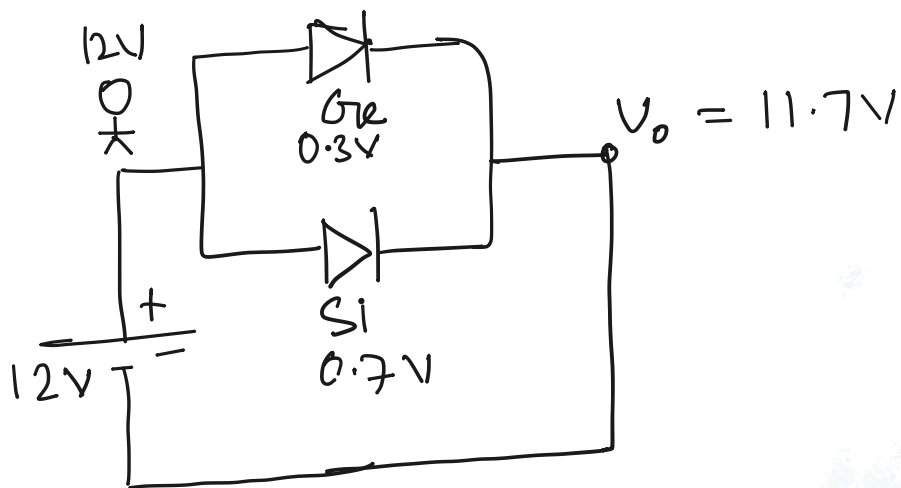


Case-2

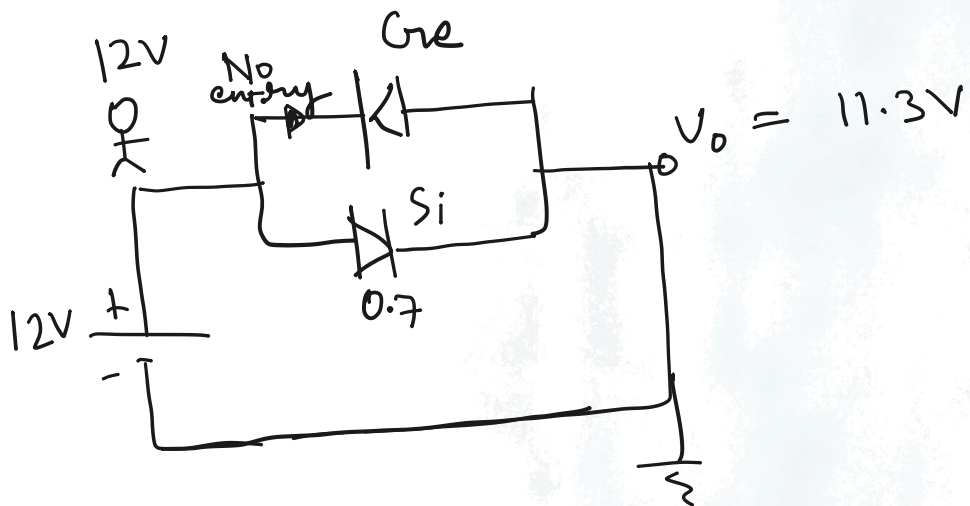

- 16** The reverse breakdown voltage of a Zener diode is 5.6 V in the given circuit. NEET

$$17 \text{ mA} = \frac{3.4}{200}$$

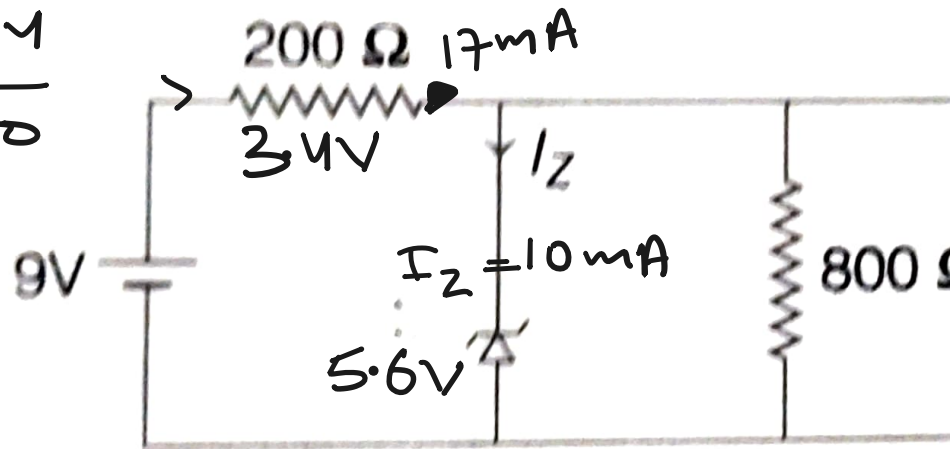


$$800 \Omega, 5.6 \text{ V}, I = \frac{5.6}{800} = 7 \text{ mA}$$

The current I_Z through the Zener is (2019 Main 8 April I)

- ✓ (a) 10 mA (b) 17 mA (c) 15 mA (d) 7 mA

17. The reading of the ammeter for a silicon diode in the given circuit is (2018 Main)

KIET

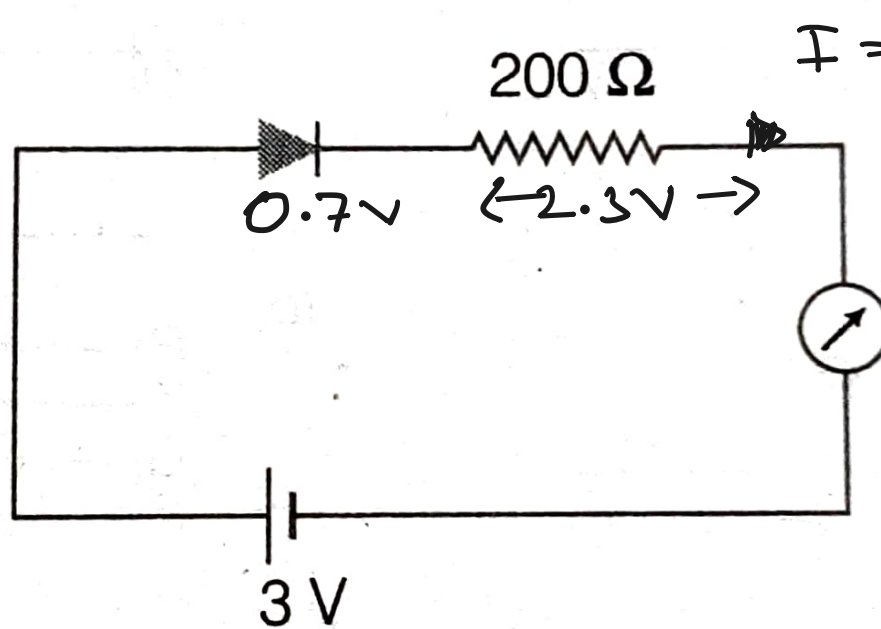

(a) 13.5 mA

(b) 0

(c) 15 mA

(d) 11.5 mA

MEET


✓ 18. In a common emitter amplifier circuit using an $n-p-n$ transistor, the ~~phase difference~~ between the input and the output voltages will be (2017 Main)

(a) 90°

(b) 135°

✓ (c) 180°





(d) 45°

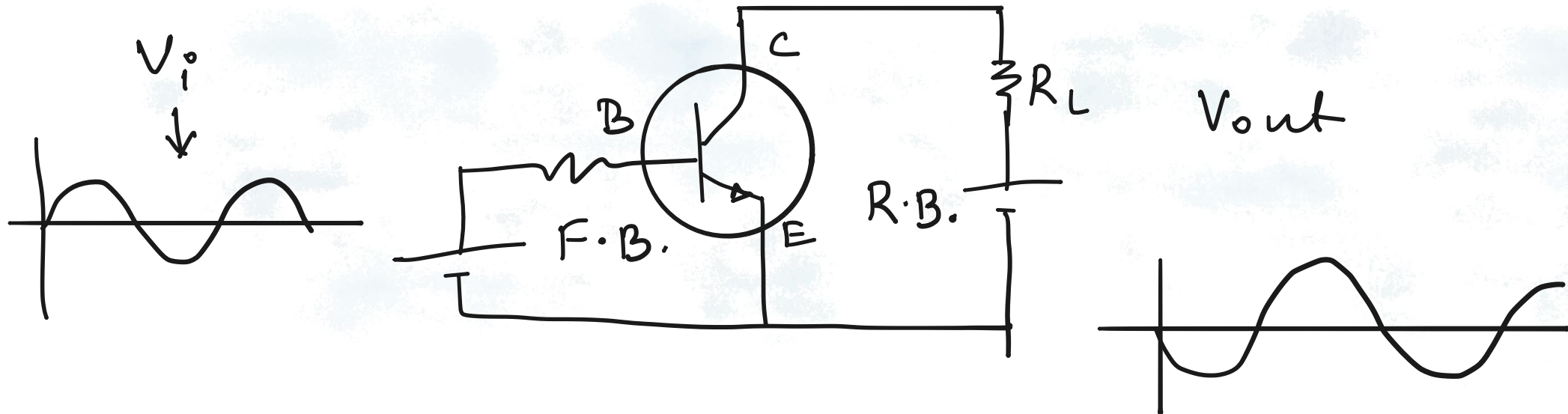

19. The temperature dependence of resistances of Cu and undoped Si in the temperature range 300-400 K, is best described by **(2016 Main)**

- (a) linear increase for Cu, linear increase for Si
- (b) linear increase for Cu, exponential increase for Si
- ✓ (c) linear increase for Cu, exponential decrease for Si
- (d) linear decrease for Cu, linear decrease for Si

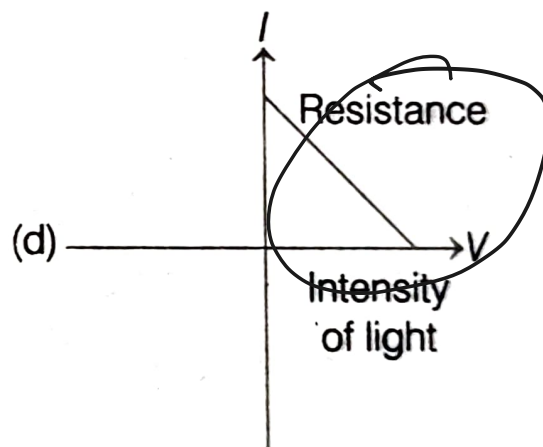
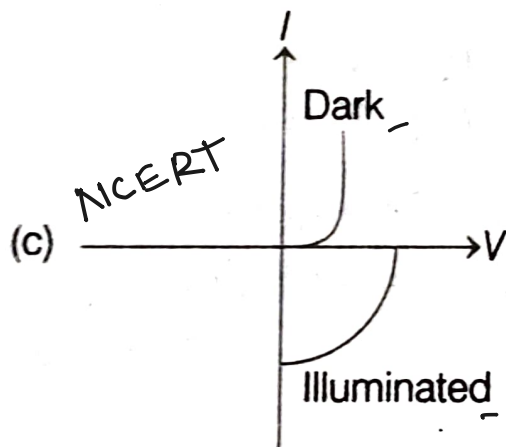
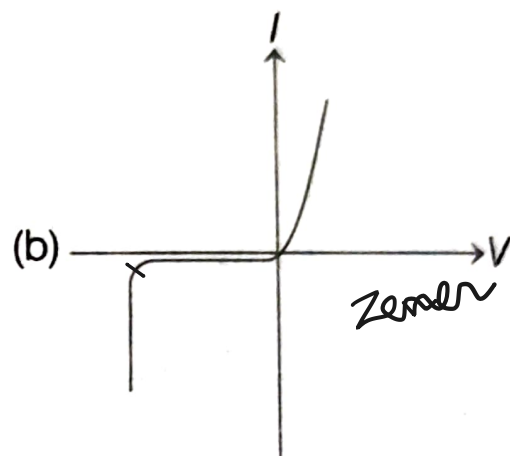
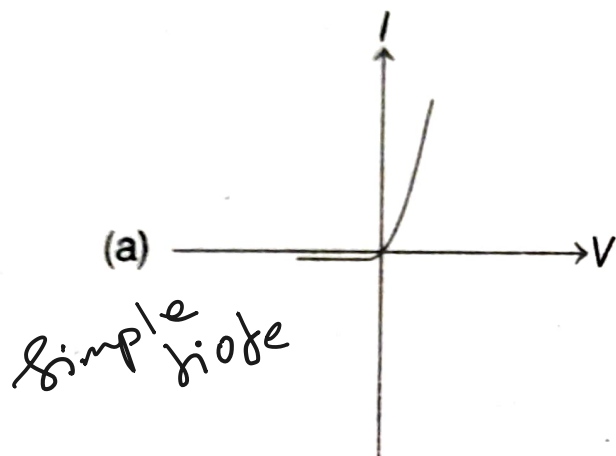
20. Identify the semiconductor devices whose characteristics are as given below, in the order (a),(b),(c),(d). **(2016 Main)**



- (a) Simple diode, Zener diode, Solar cell, Light dependent resistance
- (b) Zener diode, Simple diode, Light dependent resistance, Solar cell
- (c) Solar cell, Light dependent resistance, Zener diode, Simple diode
- (d) Zener diode, Solar cell, Simple diode, Light dependent resistance

NEET

21. The forward biased diode connection is

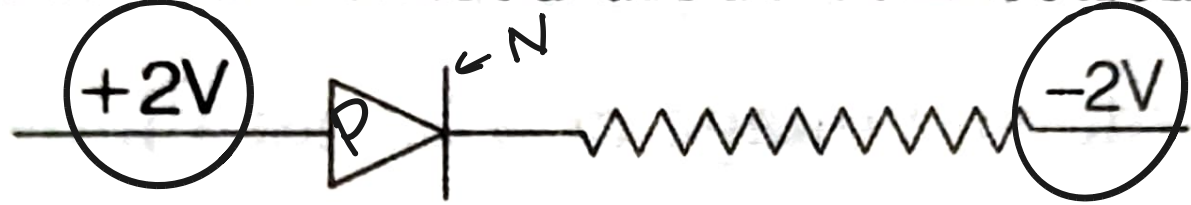
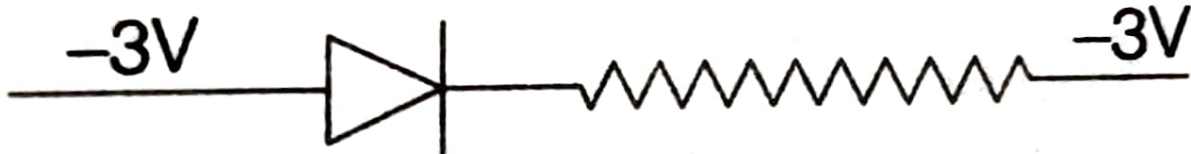
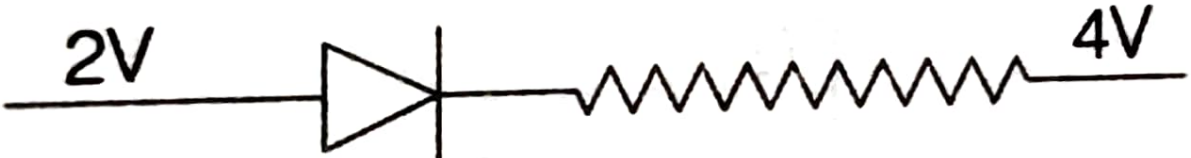
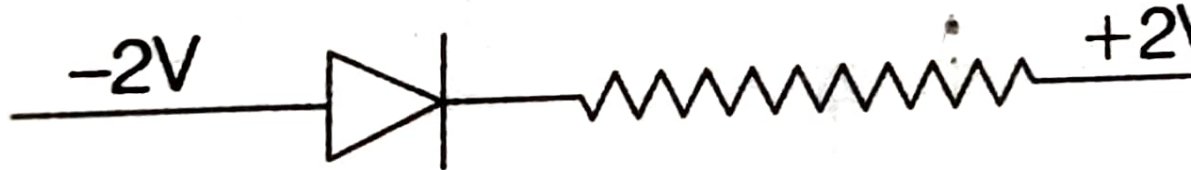
- (a) 
- (b) 
- (c) 
- (d) 

For forward bias P should be at
higher potential.

V.I.M.


22. The I - V characteristic of an LED is

(2013 Main)

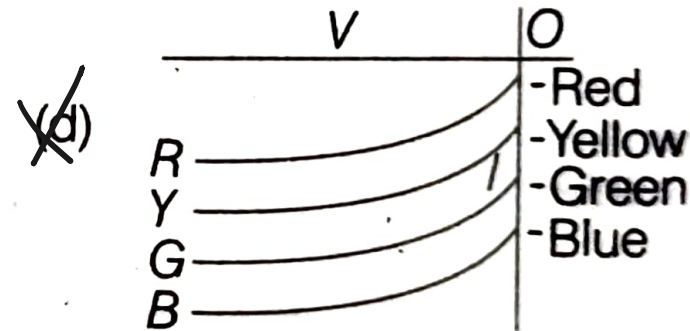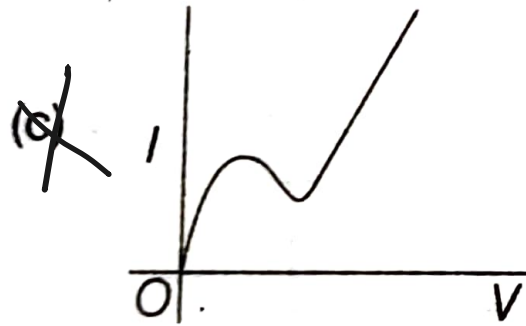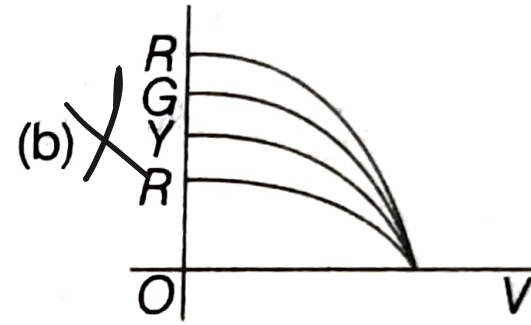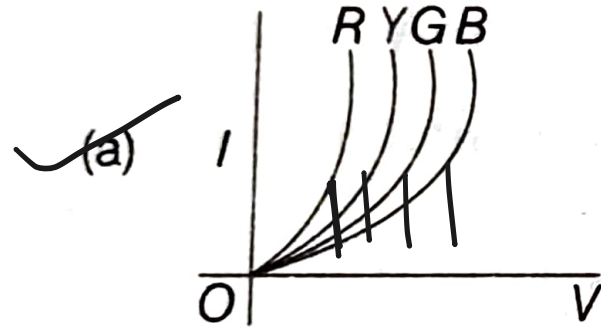





we use L.E.D. in f.B.

V
I
B
G
Y
O
R

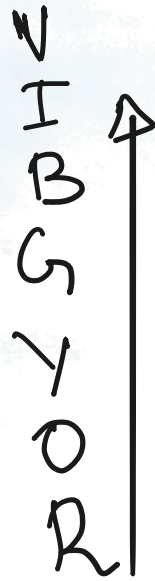

Vol. of LED when we increase
voltage

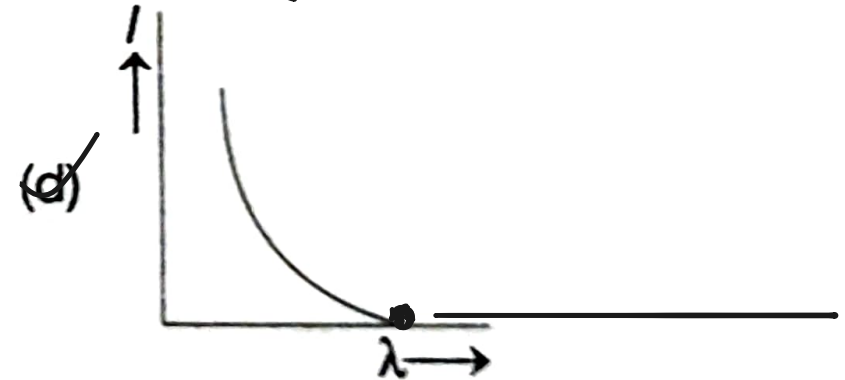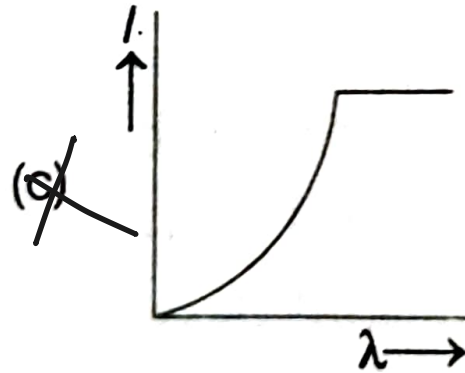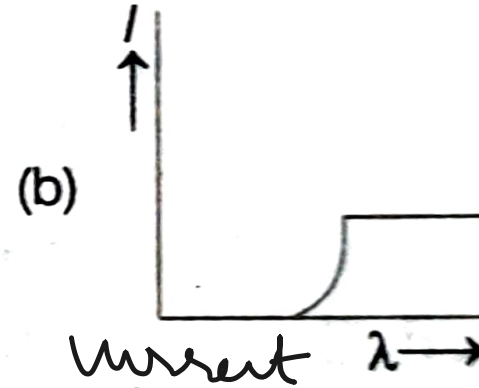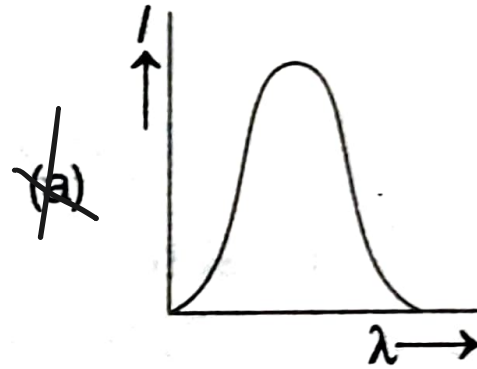- 23.** The anode voltage of a photocell is kept fixed. The wavelength λ of the light falling on the cathode is gradually changed. The plate current I of photocell varies as follows
(2013 Main)



$$\lambda \uparrow \quad \downarrow E = \frac{hc}{\lambda \uparrow}$$

24. A diode detector is used to detect an amplitude modulated wave of 60% modulation by using a condenser of capacity 250 pF in parallel with a load resistance 100 k Ω . Find the maximum modulated frequency which could be detected by it. **(2013 Main)**

(a) 10.62 MHz

(b) 10.62 kHz

(c) 5.31 MHz

(d) 5.31 kHz


25. In a p - n junction diode not connected to any circuit

(a) the potential is the same everywhere. (1998, 2M)

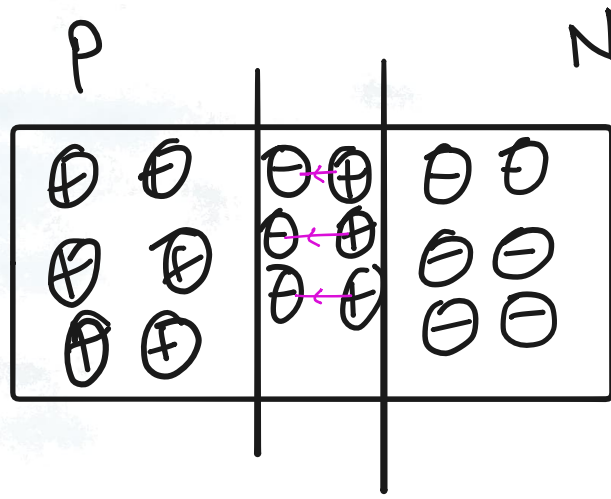(b) the p -type side is at a higher potential than the n -type side.

☒ (c) there is an electric field at the junction directed from the n -side to the p -type side.

☐ (d) there is an electric field at the junction directed from the p -type side to the n -type side.



25. In a p - n junction diode not connected to any circuit

- (a) the potential is the same everywhere. (1998, 2M)
- (b) the p -type side is at a higher potential than the n -type side.
- (c) there is an electric field at the junction directed from the n -side to the p -type side.
- (d) there is an electric field at the junction directed from the p -type side to the n -type side.

